

FPGA tutorial

Lecture 3

11.11.2020

Jochen Steinmann

How does the exam look like?

- Writing some VHDL code / just code inside the module
 - e.g. a counter etc.
- „Manual simulation“ of VHDL code
 - e.g. what does a module do?
- For sure not: Find errors in VHDL code.



Solution 2a

```
entity lecture02 is
  port(
    i_sl_CLK      : in  std_logic;           -- clock
    i_sl_en       : in  std_logic;           -- enable
    i_sl_dir      : in  std_logic;           -- direction
    o_slv_shift   : out std_logic_vector(7 downto 0) -- shift register
  );
end lecture02;


-----

architecture behavior of lecture02 is
  signal shift_reg : std_logic_vector(7 downto 0) := "00000001"; -- define signal, because we cannot readback outputs
begin

  process(i_sl_CLK)
  begin
    if rising_edge(i_sl_CLK) then
      if (i_sl_en = '1') then
        if(i_sl_dir = '1') then
          shift_reg <= shift_reg(6 downto 0) & shift_reg(7);
        else
          shift_reg <= shift_reg(0) & shift_reg(7 downto 1);
        end if;
      end if;
      o_slv_shift <= shift_reg;
    end if;
  end process;

end behavior;
```

Explanation of shift operation

 

split bus in bit 7 and rest




move bit 7 to right position

←
shift direction

Solution 2a

Simulation output

 

Solution 2b

Counter

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

-----

entity counter is
    port(
        i_sl_CLK      : in  std_logic;           -- clock
        i_sl_en       : in  std_logic;           -- enable
        i_sl_dir       : in  std_logic;           -- direction
        o_slv_counter : out std_logic_vector(7 downto 0) -- counter
    );
end counter;

-----

architecture behavior of counter is
    signal cnt : unsigned(7 downto 0) := (others => '0'); -- define signal, because we cannot readback outputs
begin

    process(i_sl_CLK)
    begin
        if rising_edge(i_sl_CLK) then
            if (i_sl_en = '1') then
                if(i_sl_dir = '0') then
                    cnt <= cnt + 1;
                else
                    cnt <= cnt - 1;
                end if;
            end if;
            o_slv_counter <= std_logic_vector(cnt);
        end if;
    end process;

end behavior;
```

Solution 2b

Alternative solution – same result

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

-----

entity counter is
  port(
    i_sl_CLK      : in  std_logic;           -- clock
    i_sl_en       : in  std_logic;           -- enable
    i_sl_dir      : in  std_logic;           -- direction
    o_slv_counter : out std_logic_vector(7 downto 0) -- counter
  );
end counter;

-----


architecture behavior of counter is
  signal cnt : std_logic_vector(7 downto 0) := (others => '0'); -- define signal, because we cannot readback outputs
begin

  process(i_sl_CLK)
  begin
    if rising_edge(i_sl_CLK) then
      if (i_sl_en = '1') then
        if(i_sl_dir = '0') then
          cnt <= std_logic_vector(unsigned(cnt) + 1);
        else
          cnt <= std_logic_vector(unsigned(cnt) - 1);
        end if;
      end if;
      o_slv_counter <= cnt;
    end if;
  end process;

end behavior;
```


Solution 2b


Simulation output

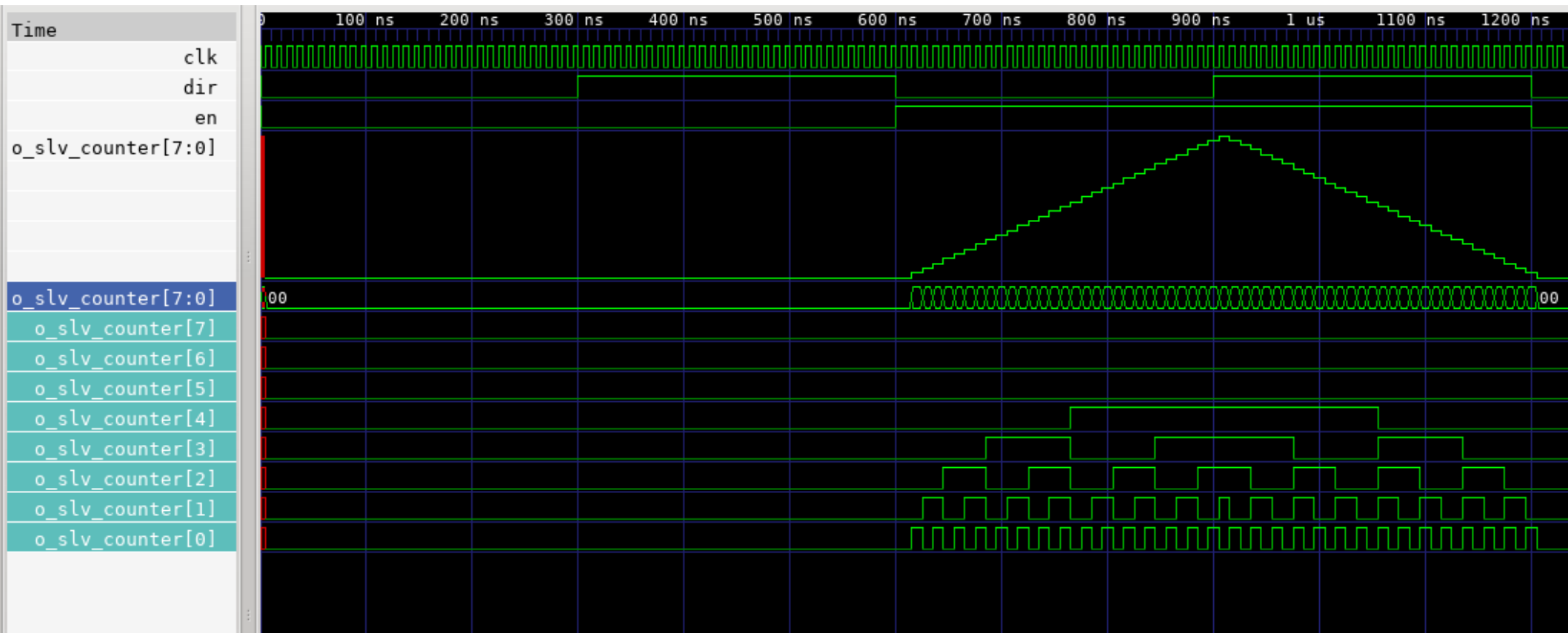

NEW

- Inside the FPGA everything is executed in parallel!
- It does not matter in which line the definition is written.
 - Order just matters inside one Block

Scope of VHDL

 

Reusing VHDL code

- We have written an 8 bit counter
 - What, if we want a different bit size?
 - rewrite the whole code?
 - Create counter_8bit, counter_9bit, counter_32bit, counter_3bit?

- Use **generic**

```
entity counter is
  generic (
    data_width : integer := 8
  );
  port (
    i_sl_clk      : in  std_logic;
    o_slv_counter : out std_logic_vector(data_width-1 downto 0)
  );
end counter;
```

integer is just a number

- Generics have to appear in the component and generic map

Changing generic

```
COMPONENT counter is
  generic(
    DATA_WIDTH : integer := 8
  );
  port(
    i_sl_CLK      : in  std_logic;           -- clock
    i_sl_en       : in  std_logic;           -- enable
    i_sl_dir       : in  std_logic;           -- direction
    i_sl_rst       : in  std_logic;           -- reset
    o_slv_counter : out std_logic_vector(DATA_WIDTH-1 downto 0) -- counter
  );
end COMPONENT;
```

```
-- Instance of unit under test.
 uut: counter
  PORT MAP (
    i_sl_CLK      => CLK,
    i_sl_en       => en,
    i_sl_dir       => dir,
    i_sl_rst       => rst,
    o_slv_counter => o_slv_counter
  );

 uut2: counter
  GENERIC MAP(
    DATA_WIDTH => 9
  )
  PORT MAP (
    i_sl_CLK      => CLK,
    i_sl_en       => en,
    i_sl_dir       => dir,
    i_sl_rst       => rst,
    o_slv_counter => o_slv_counter2
  );
```

Comparing two values

- If we want to compare two values, we have to use ,signed‘ or ,unsigned‘

if unsigned(slv_pwm_cnt) >= unsigned(i_slv_val) then

Works just in if clause, means, we cannot assign the values to a signal directly

Constants

Sometimes, things are really constant

- For example the data_width in a testbench

```
constant DATA_WIDTH : integer := 4;
```



like #define in C / C++

Resetting a module

- There are a two ways how to reset a module:
 - **Asynchronous reset**
 - Reset signal can be raised without any relation to the clock
 - **Synchronous reset**
 - Reset signal is evaluated on clock event
- A FPGA is made for a synchronous reset
 - Relates on the internal structure of the logic blocks


Creating analog outputs

  - Needed for
 - thresholds
 - stimulus waveforms
 - testpulses




1-Pin DAC

 - Pulse-Width-Modulation
PWM
- Pulse Density Modulation
PDM
 - Delta-Sigma-DAC




 Example for PDM Sigma-Delta-DAC
same Pulsewidth but different Pulses per time!




Real analogue output

 - PWM needs some smoothing
 - for normal low-pass filter is sufficient (here 2nd order)




PWM to Volts

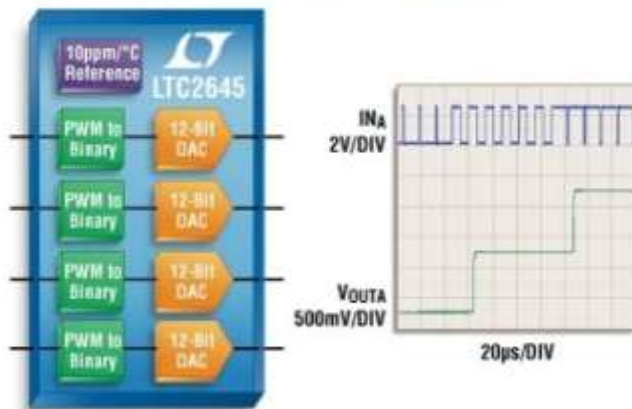


- not very linear
 - but this can be solved by calibration

Creation of different pulse width

 


Average

 

PWM Period: Time until counter overrun.

 Output: Comparison between counter and setpoint



Compare Counter

How to use a module in a module?

- COMPONENT direct after architecture

```
architecture behavior of pwm is
  COMPONENT counter is
    generic(
      DATA_WIDTH : integer := 8
    );
    port(
      i_sl_CLK      : in  std_logic;           -- clock
      i_sl_en       : in  std_logic;           -- enable
      i_sl_dir      : in  std_logic;           -- direction
      i_sl_rst      : in  std_logic;           -- reset
      o_slv_counter : out std_logic_vector(DATA_WIDTH-1 downto 0) -- counter
    );
  end COMPONENT;

  signal slv_pwm_cnt : std_logic_vector(DATA_WIDTH-1 downto 0) := (others => '0');
```

- PORT MAP as done in testbench

ToDo for today...

- **3a:** Implement generics in your counter
 - one 8 bit and one 9 bit counter
- **3b:** Implement a reset in your counter
- **3c:** Implement a first version of the PWM by using counter
 - Use your counter and skeleton3c.zip from MOODLE

starting point, solution 2b