

FPGA tutorial

Lecture 4

18.11.2020

Jochen Steinmann



Solution 03a

Counter with GENERIC

```
entity counter is
  generic(
    DATA_WIDTH      : integer := 8
  );
  port(
    i_sl_CLK         : in  std_logic;           -- clock
    i_sl_en          : in  std_logic;           -- enable
    i_sl_dir         : in  std_logic;           -- direction
    o_slv_counter    : out std_logic_vector(DATA_WIDTH-1 downto 0) -- counter
  );
end counter;

-----

architecture behavior of counter is
  signal cnt : unsigned(DATA_WIDTH-1 downto 0) := (others => '0'); -- define signal, because we cannot readback outputs
begin

  process(i_sl_CLK)
  begin
    if rising_edge(i_sl_CLK) then
      if (i_sl_en = '1') then
        if(i_sl_dir = '0') then
          cnt <= cnt + 1;
        else
          cnt <= cnt - 1;
        end if;
      end if;
      o_slv_counter <= std_logic_vector(cnt);
    end if;
  end process;

end behavior;
```

Testbench

```
BEGIN
  -- Instance of unit under test.
  uut: counter
  PORT MAP (
    i_sl_CLK    => CLK,
    i_sl_en     => en,
    i_sl_dir    => dir,
    o_slv_counter => o_slv_counter
  );

  uut2: counter
  GENERIC MAP(
    DATA_WIDTH => 9
  )
  PORT MAP (
    i_sl_CLK    => CLK,
    i_sl_en     => en,
    i_sl_dir    => dir,
    o_slv_counter => o_slv_counter2
  );

  -----

  -- test bench definition.
  tb_CLK :process
  begin
    CLK <= '0';
    wait for 1 ns;
    CLK <= '1';
    wait for 1 ns;
  end process;

END;
```

Solution 03 a

ads



Solution 03b

Counter with RESET

```
architecture behavior of counter is
    signal cnt : unsigned(DATA_WIDTH-1 downto 0) := (others => '0'); -- define signal, because we cannot readback outputs
begin

    process(i_sl_CLK)
    begin
        if rising_edge(i_sl_CLK) then
            if (i_sl_en = '1') then
                if (i_sl_rst = '1') then
                    cnt <= (others => '0');
                else
                    if(i_sl_dir = '0') then
                        cnt <= cnt + 1;
                    else
                        cnt <= cnt - 1;
                    end if;
                end if;
            elsif (i_sl_rst = '1') then
                cnt <= (others => '0');
            end if;
            o_slv_counter <= std_logic_vector(cnt); -- option 1a ( o_slv_counter is always 1 clock cycle late related to cnt )
        end if;
        o_slv_counter <= std_logic_vector(cnt); -- option 1b ( o_slv_counter is always 1 clock cycle late related to cnt )
    end process;


    -- o_slv_counter <= std_logic_vector(cnt); -- option 2 ( o_slv_counter and cnt have the same value at the same clock cycle)

end behavior;
```

```
entity counter is
    generic(
        DATA_WIDTH : integer := 8
    );
    port(
        i_sl_CLK      : in  std_logic;           -- clock
        i_sl_en       : in  std_logic;           -- enable
        i_sl_dir      : in  std_logic;           -- direction
        i_sl_rst      : in  std_logic;           -- reset
        o_slv_counter : out std_logic_vector(DATA_WIDTH-1 downto 0) -- counter
    );
end counter;
```

Solution 03 b

asd

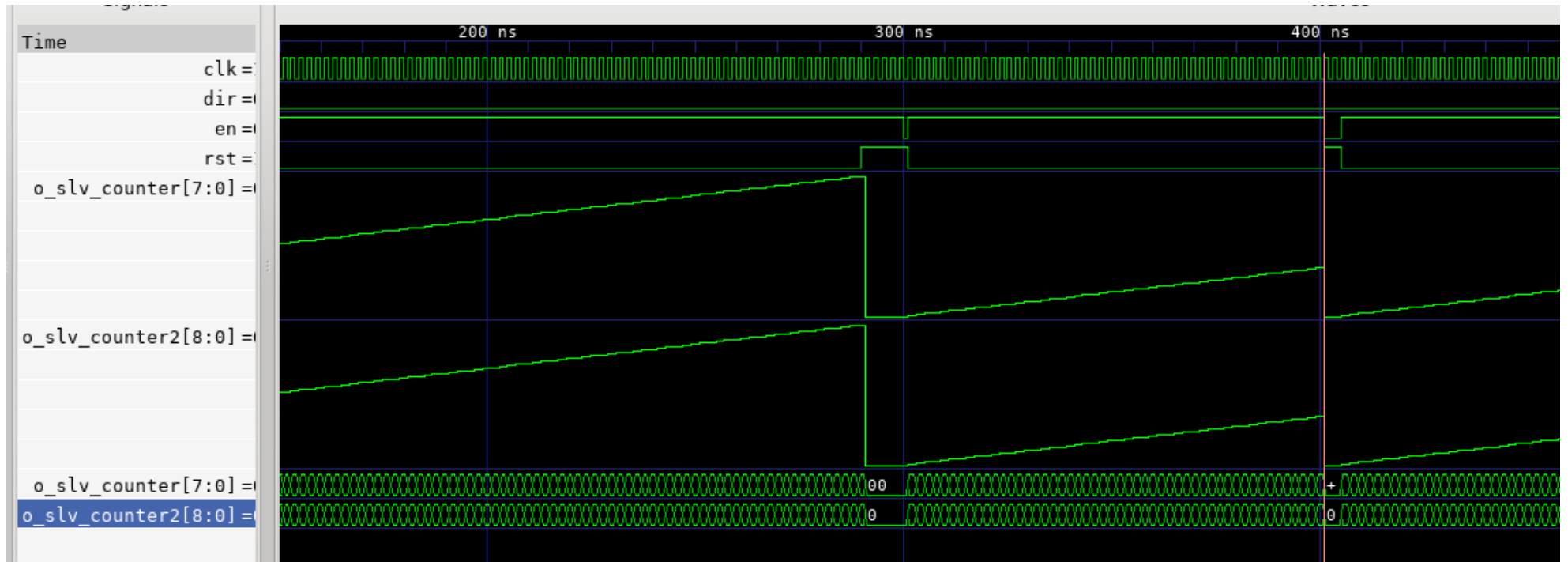


A short look, where to assign the outputs

Inside CLK process or outside


- Option 01 inside CLK process
 - Rising edge

Output delayed by 1 clock cycle

 

- No rising edge


Output delayed by 0.5 clock cycle

 

Action on falling edge
– should be avoided

- Option 02 outside CLK process

Output delayed by 0 clock cycle

 

Solution 03c

```
entity pwm is
  generic(
    DATA_WIDTH      : integer := 8
  );
  port(
    i_sl_CLK         : in  std_logic;           -- clock
    i_slv_val        : in  std_logic_vector(DATA_WIDTH-1 downto 0); -- pwm value
    o_sl_pwm         : out std_logic           -- pwm output
  );
end pwm;

signal slv_pwm_cnt : std_logic_vector(DATA_WIDTH-1 downto 0) := (others => '0');

begin
  pwm_cnt: counter
  GENERIC MAP(
    DATA_WIDTH => DATA_WIDTH
  )
  PORT MAP (
    i_sl_CLK    => i_sl_clk,
    i_sl_en     => '1',
    i_sl_dir    => '0',
    i_sl_rst    => '0',
    o_slv_counter => slv_pwm_cnt
  );

  process(i_sl_CLK)
  begin
    if rising_edge(i_sl_CLK) then
      if unsigned(slv_pwm_cnt) >= unsigned(i_slv_val) then
        o_sl_pwm <= '0';
      else
        o_sl_pwm <= '1';
      end if;
    end if;
  end process;

end behavior;
```

Solution 03 c


PWM



You might have seen some warning like this:

```
../src/ieee2008/numeric_std-body.vhdl:1624:7:@1ns:(assertion warning): NUMERIC_STD.">=": metavalue detected, returning FALSE
```

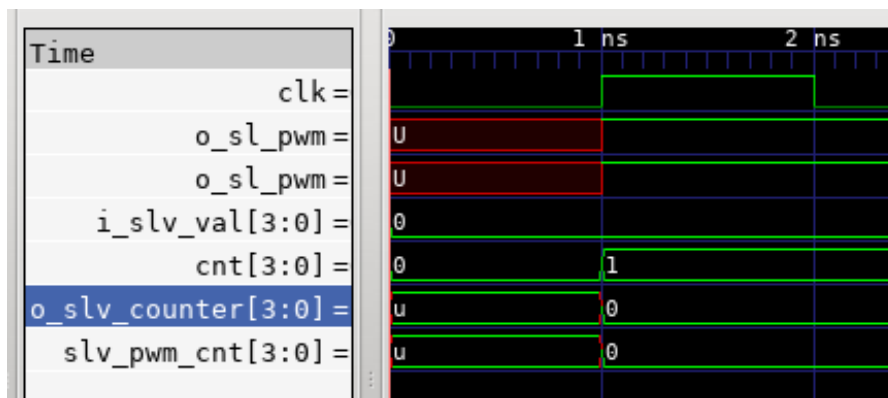At the beginning there is (depending on the implementation) a short time of undefined:



NEW

VHDL

for loop

For writing testbenches or even some algorithms, sometimes, it is useful to use loops

```
for I in 0 to 3 loop
    if (A = I) then
        Z(I) <= '1';
    end if;
end loop;
```

There is no need to define the loop parameter (e.g. I)

Calculation with GENERIC

- Sometimes, you have to give certain values, which rely on each other
- As an example, you have to constrain the vector width and the numbers
 - Let's assume BIT_WIDTH is 3
 - `std_logic_vector(BIT_WIDTH -1 downto 0)` 3 bit (2 – 0)
 - `std_logic_vector((2** BIT_WIDTH) -1 downto 0)` $2^3 = 8$ bit (7 – 0)

- Also case is quite useful, when we want to build some logic

```
C2: case y is
    when "00" => Out_2 <= 0;
    when "01" => Out_2 <= 1;
    when others => Out_2 <= 3; -- would be "10" and "11"
end case C2;
```

CASE input IS

WHEN "00" =>


```
    output0 <= '1' ;
    output1 <= '0' ;
    output2 <= '0' ;
    output3 <= '0' ;
```

Multiple „actions“ are also possible

Excercises

Talking to many devices

 - Address decoder
- selects only one device
3 out of 8
- 2 different types
 - one hot (1)
 - one cold (0)
- all others inverted logic level



one famous type:
74 HC 138

Logic table of 74HC138

FUNCTION TABLE

ENABLE INPUTS			SELECT INPUTS			OUTPUTS							
G1	$\overline{G2A}$	$\overline{G2B}$	C	B	A	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7

disabled

L	L	L	L	H	H	H	H	H	H	H	H	H	H
L	L	H	H	L	H	H	H	H	H	H	H	H	H
L	H	L	H	H	L	H	H	H	H	H	H	H	H
L	H	H	H	H	H	L	H	H	H	H	H	H	H
H	L	L	H	H	H	H	L	H	H	H	H	H	H
H	L	H	H	H	H	H	H	L	H	H	H	H	H
H	H	L	H	H	H	H	H	H	L	H	H	H	H
H	H	H	H	H	H	H	H	H	H	H	L	H	H
H	H	H	H	H	H	H	H	H	H	H	H	L	H
H	H	H	H	H	H	H	H	H	H	H	H	H	L

Need of an address decoder?

- Independent:
 - outside FPGA
 - inside FPGA
- Different logic blocks (chips) have to be addressed.
 - ensure that only one is active and talks with the master
 - if multiple devices (slave) are active, may cause short circuits and lot of trouble

Exercise 12

- Address encoder

- if talking to multiple chips, you have to ensure, that only one is selected at the same time!
- Two options
 - one hot → selected chip 1, others 0
 - one cold → selected chip 0, others 1
- Input
 - 2 bit (0-3)
- Output
 - 4 bit


Hint:

**you can use a bus to access elements of a bus
 $a[b]$ → will access the bit b of a**

- There are many ways how an FPGA device can communicate with the “operator”
 - High energy physics
 - mostly remote access → e.g. Network etc.
 - Consumer devices
 - need graphical menues
 - LEDs → easy
 - **7-Segment displays → more complex, but still simple**
 - LCDs → too complex for this course

Difference

 - Humans use **decimal** system
- FPGAs and computers use **binary** system
- Need to convert between different worlds
 - $1001 \rightarrow 9$




1st 7 segment lookup table

Exercise 13

- Heading forwards to display numbers on the 7-segement display
- Lookup table for 7 segment display
 - 7 segments can display 10 values 0 – 9
 - depending on the input different outputs have to be switched on
- Inputs 4 Bit \rightarrow sw3 – sw0
- Outputs 8 Bit \rightarrow 7 Segments

Exercise 13


 


An un-illuminated seven-segment display, and nine illumination patterns corresponding to decimal digits


one Bus
segments = “0000011”;
A + B on

Exercise 13

Pin 1

  

Multiplexing

 

<u>SEL1</u>	<u>SEL0</u>	<u>OUT</u>
0	0	0
0	1	1
1	0	2
1	1	3

Exercise 14

- Create a 16 bit (= 4 x 4bit) to 4bit multiplexer
- Inputs
 - sel 2 bit, which select which part of the input is “connected” to the output
 - in 16 bit
 - out 4 bit

04a address decoder

(de-) select one bit of 8

3 bit input

3 to 8 (one cold)

3 to 8 (one hot)

04b 7 segment lookup table

map 4 input bits to the 7 segments, which
should light up

use case - structure

04c Multiplexer

Multiplex 4 x 4bit to 1 x 4 bit depending on the selected input

Have a look into the skeletons folder